
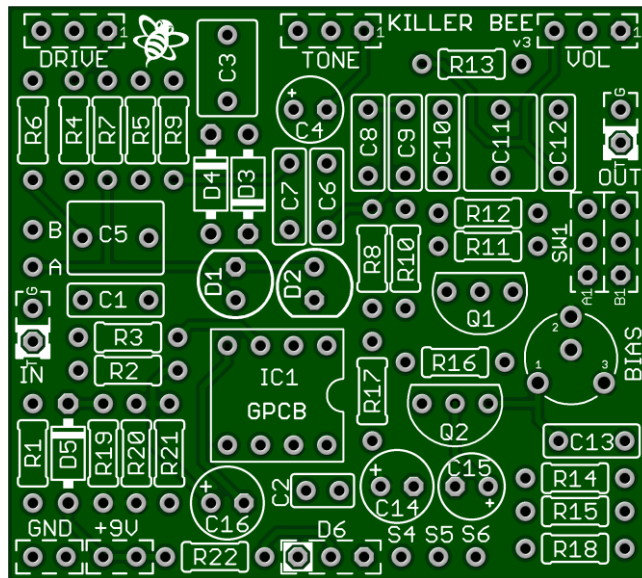


Killer Bee

This is the famous low to medium gain circuit with some modern features. Use this in front of an overdriven tube amp and push your amp into distortion or run it in tandem with other dirt pedals. All the sweet sound you would expect but what makes our version “Killer” is the addition of a foot switchable boost for more sustain and volume. Instantly add more gain and sustain under either setup than could be achieved using a similar circuit and still have the ultimate in touch sensitive expression.

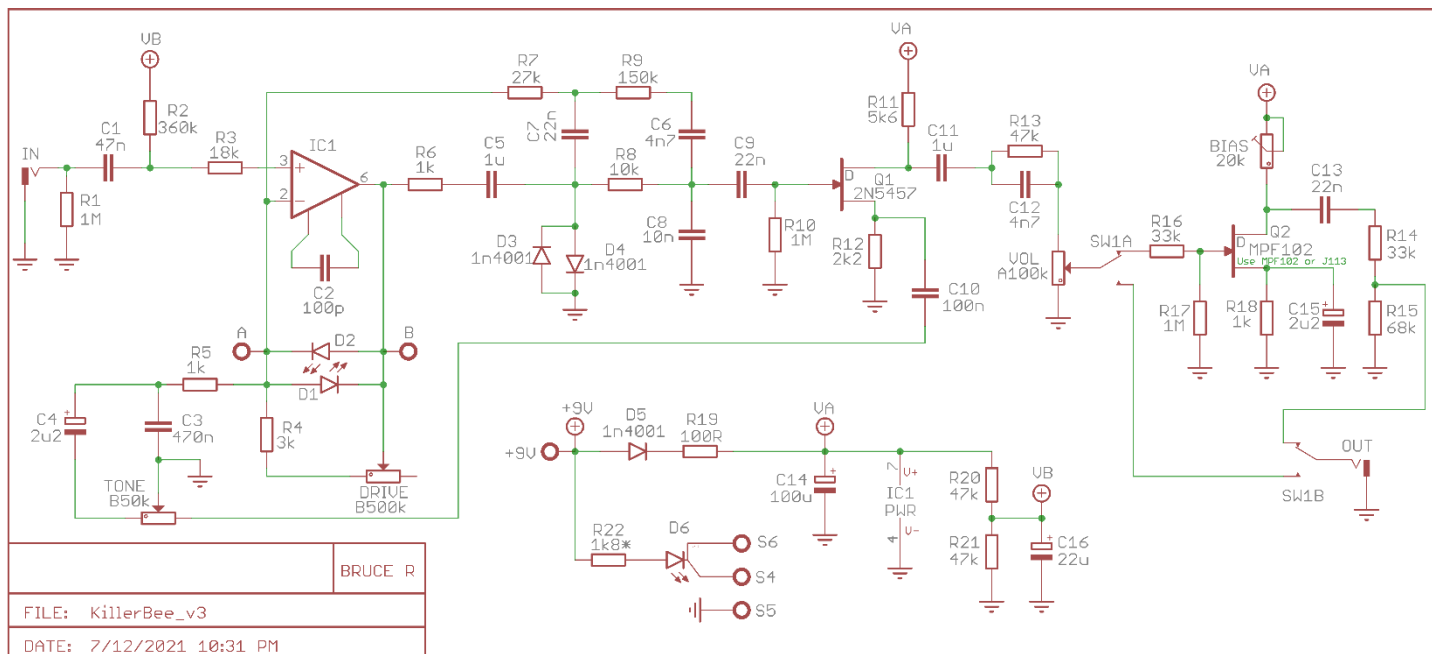

Part	Value	Part	Value	Part	Value	Part	Value
R1	1M	R16	33k	C8	10n	VOL	A100K
R2	360k	R17	1M	C9	22n	DRIVE	B500K
R3	15k	R18	1k	C10	100n	BIAS	20K
R4	3k	R19	100R	C11	1u	TONE	B50K
R5	1k	R20	47k	C12	4n7		
R6	1k	R21	47k	C13	100n	Switch	** DPDT
R7	27k	R22	1k8	C14	100u		
R8	10k			C15	22u	IC1	* TL071
R9	150k	C1	47n	C16	22u	Q1	2N5457
R10	1M	C2	100p			Q2	*** J113
R11	5k6	C3	220n	D1	LED		
R12	2k2	C4	2u2	D2	LED	D6	Status LED
R13	47k	C5	1u	D3	1n4001		
R14	33k	C6	4n7	D4	1n4001		
R15	68k	C7	22n	D5	1n4001		



Build Notes:

* Use TL071, CA3130, NE5534 or other Mono Opamps. If you use CA3130, populate C2. If you use either of the other two choices suggested C2 is not needed and can be simply left off the board.

** We recommend the use of a DPDT foot switch although you may use a toggle. By using a footswitch, you have much more flexibility. You may also use a 3PDT in order to add an LED to the switch.

*** While J113 is an excellent choice a N.O.S. MPF102 is equivalent. The orientation for both is identical to the silkscreen on the board. Both should be biased at approximately 6 volts on the drain leg to ground. Be very careful not to purchase counterfeit FETs from eBay, Amazon or similar. Kits may come with either genuine transistor.

A / B Pads: The DPDT Wiring Board above is an optional mod. Use the DPDT wiring board to load your own favorite combination of clipping options and simply do not install D1 and D2.

Mods are typically not included with KITS.

Controls:

Drive: Turn clockwise for more overdrive.

Tone: Turn clockwise for a brighter tone.

Volume: Turn Clockwise for more Volume


Trimmer: Bias the drain (or D) leg of J113 or (MPF102) using a Digital Multimeter to about 6 volts.

When biasing simply put the red probe on the (D) or drain leg, black probe on any ground, supply the circuit with (9) volts power and use the trimmer to dial in the correct voltage.

J113




STATUS LED

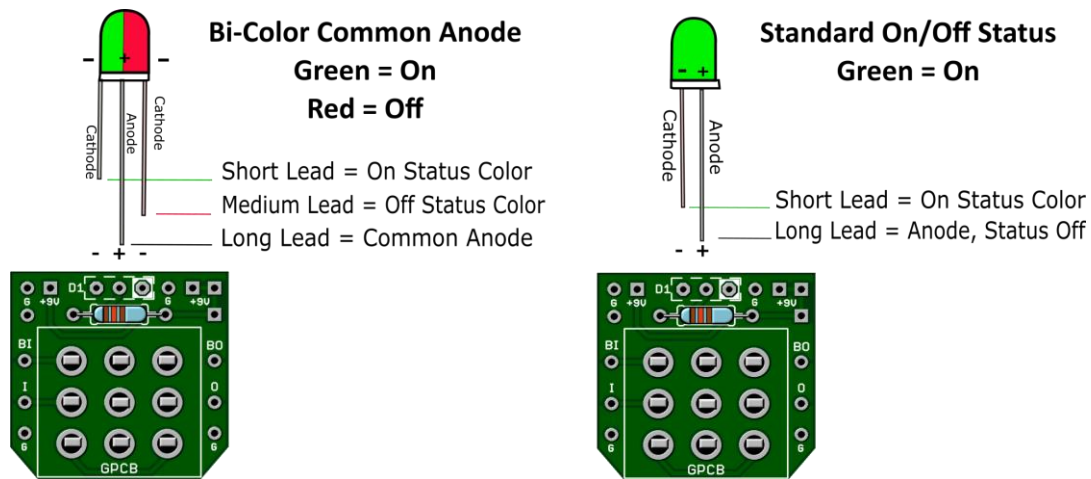

If you are using one of GuitarPCB handy 3PDT wiring boards, pads S4, S5, S6 and D6 would be ignored and R22 would not be installed. See wiring guide below for reference.


Wiring Diagram (no status LED) on Boost switch SW1:

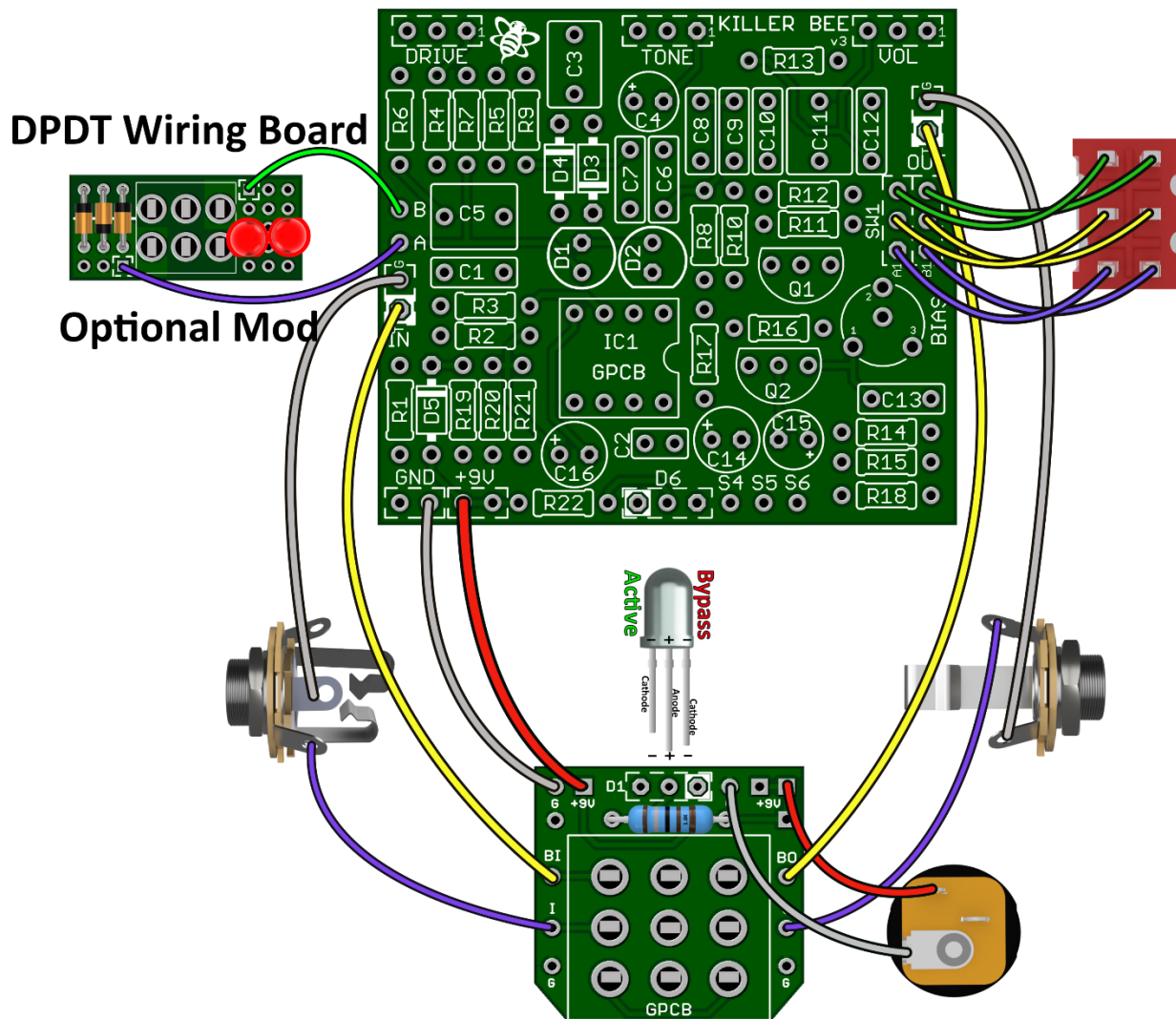The DPDT Wiring Board above is an optional mod.





Wiring Diagram (w/ status LED) on Boost switch SW1:

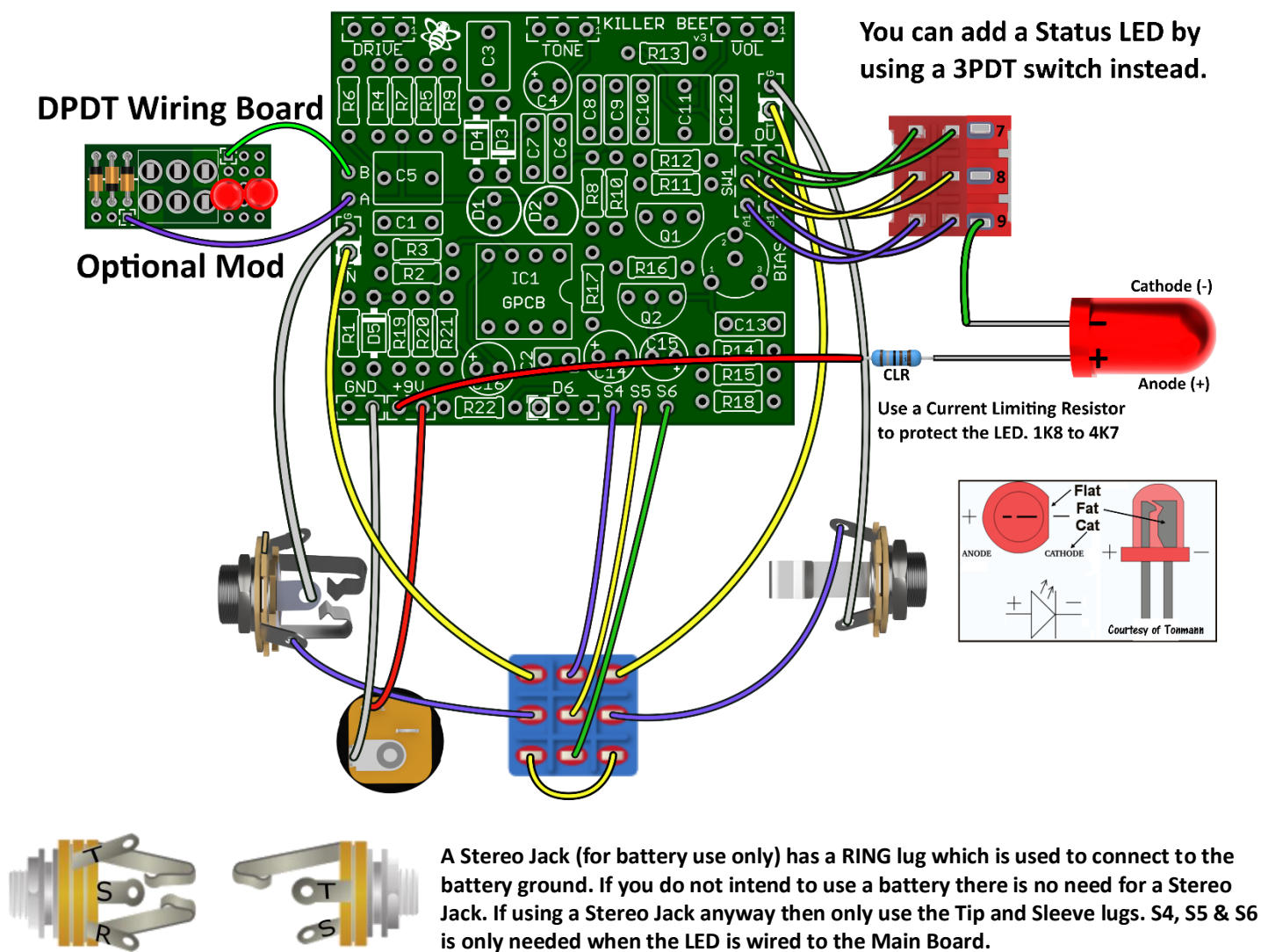The DPDT Wiring Board above is an optional mod.




KILLER BEE BOOST POT MOD

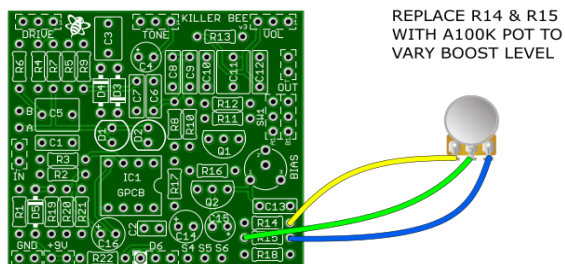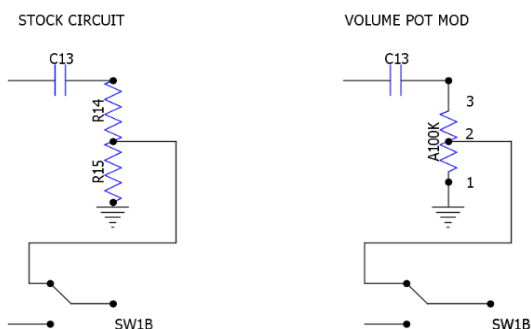



Adding a 100K Volume pot to control the amount of Boost you want. Anything below 1:00 will attenuate. Important: If you have the boost pot set too low you will not have enough volume over unity when in boost mode. Mod courtesy of Wilkie1.







GuitarPCB Tip Sheet

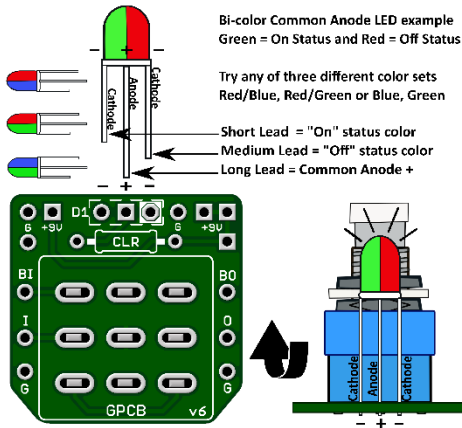

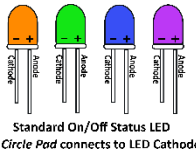
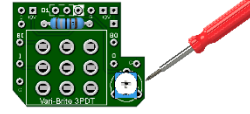
Try our 3PDT Vari-Bright version w/ on-board Trimmer to adjust brightness



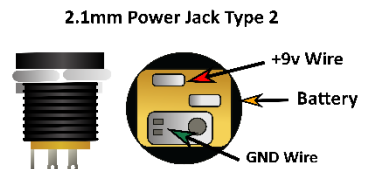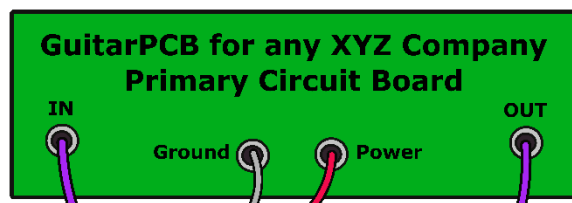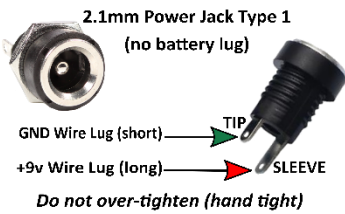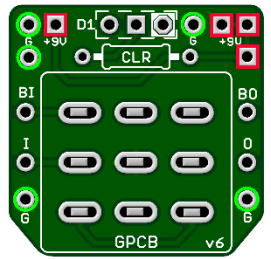- Green = Ground Pads (5)
- Red = +9v Power Pads (4)
- D1 = LED Pads
- CLR = Current Limiting Resistor
- BI = From Main Board IN
- BO = From Main Board OUT
- I = To Jack Tip IN
- O = To Jack Tip OUT




T = Tip
R = Ring
S = Sleeve

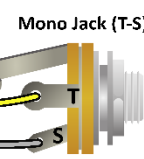
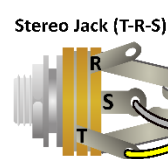


T = Tip
S = Sleeve

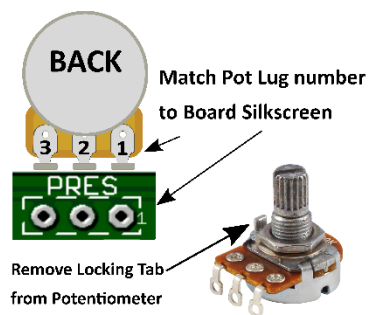
Multiple +9v and Ground Pads are convenient hookup points for additional circuits within the same enclosure. This also allows for diverse wiring schemes to suit individual needs.



Sockets make troubleshooting easier

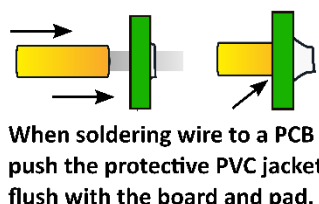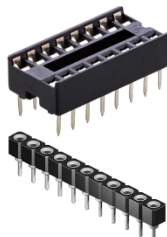

Main Board IN/OUT Pads

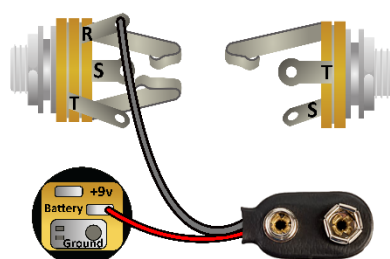

Input/Output Jack Wiring

T = Tip | R = Ring | S = Sleeve

A Stereo Jack is only needed if using a Battery. Otherwise use a Mono Jack
 Battery Strap RED wire is connected to Power Jack
 Battery Strap Black wire is connected to RING (stereo jack)
 If wiring an LED to our 3PDT Wiring Board then S4, S5 & S6 are not needed



This Build Document, PCB, Artwork and Schematic image are property of ©GuitarPCB.com
 All copyrights, trademarks and artworks remain the property of their owners.
 Any company or product names used are for identification and educational purposes only.
 GuitarPCB is in no way affiliated with any said companies and are not to be misrepresented.