


P.U.T.B. - TONEBENDER MKII PNP uses Charge Pump

The Classic Tonebender with a modern twist.

Pump'd Up means you can use it with other negative-ground pedals.

This re-designed board fits in a 1290NS/1590B or larger enclosure.

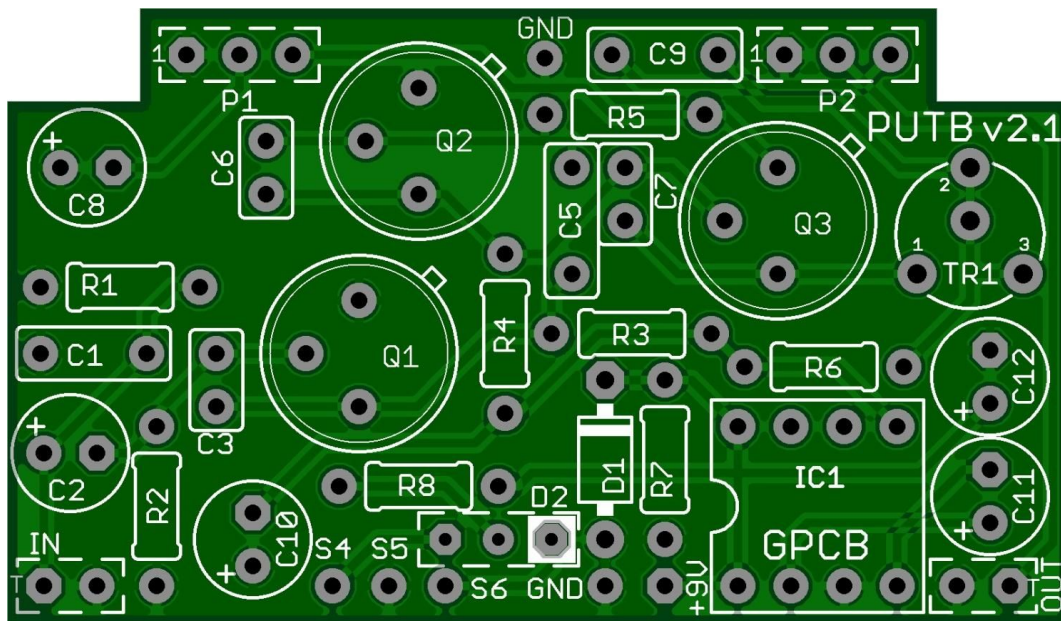
Because PNP fuzzes are positive-ground circuits, they must have a separate power supply from the rest of the effects in a chain. To overcome this limitation, a charge pump chip has been integrated to allow this board to be powered by the same source as all of your other effects. This is great for daisy-chained pedal boards, as well as integrating this into an enclosure with other effects circuits.



Board Dimensions (W x H): 2" x 1.16" i.e.: 29 x 51mm

Part	Value
R1	1M
R2	100K
R3	10K
R4	100K
R5	100K
R6	470R
R7	1M
R8	3K3
D1	1n4001
D2	Bi-Color LED Comm. Anode
TR1	20K
C1	10n
C2	4u7
C3	220p


Part	Value
C5	100n
C6	220p
C7	220p
C8	4u7
C9	10n
C10	47u
C11	10u
C12	47u
Q1	PNP
Q2	PNP
Q3	PNP
IC1	MAX1044
P1 - Attack	B1K
P2 - Level	A100K

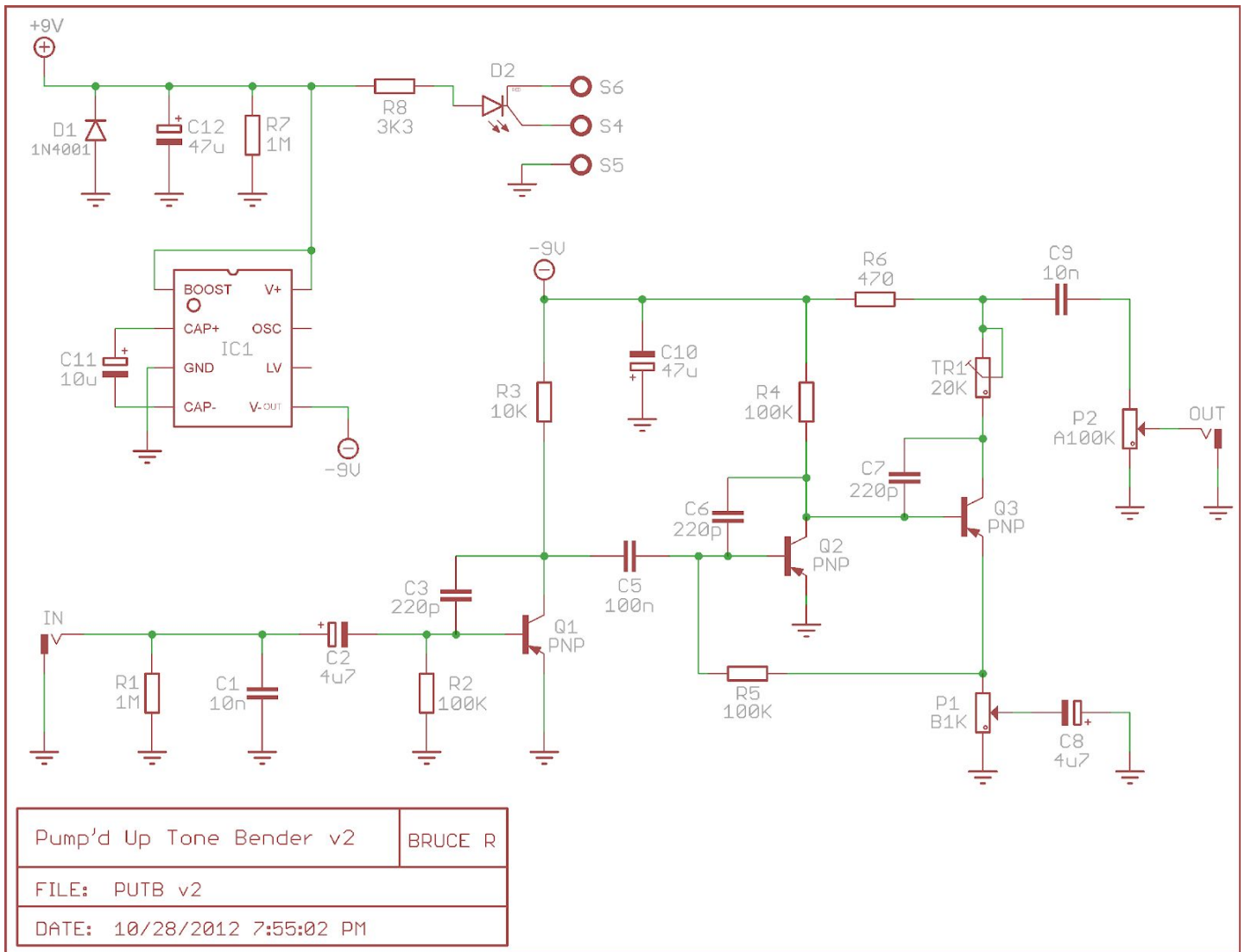

Biasing

In order to have this circuit sound like a Tone Bender, you must use transistors in the recommended gain (hFE) ranges and bias the circuit. There is a 20K trimmer potentiometer on this board designed to help you adjust the bias. Using your digital multimeter (DMM), measure the voltage between ground and the collector pin of Q3, and turn the trimmer to the right until your DMM reads around -7V. The board layout has each pin of the transistors marked if you look closely enough (zoom in or print this document). The bias can be adjusted up or down by a volt or so to your personal liking. There have been reports of some original vintage tone benders having the bias as high as -8.5V, while other germanium fuzz pedals like the fuzz face were biased at around -4.7V. In addition to a slight change to the tone, a larger negative bias value will increase the circuit's output level, which may factor into where you decide to set the bias.

Wiring Diagram

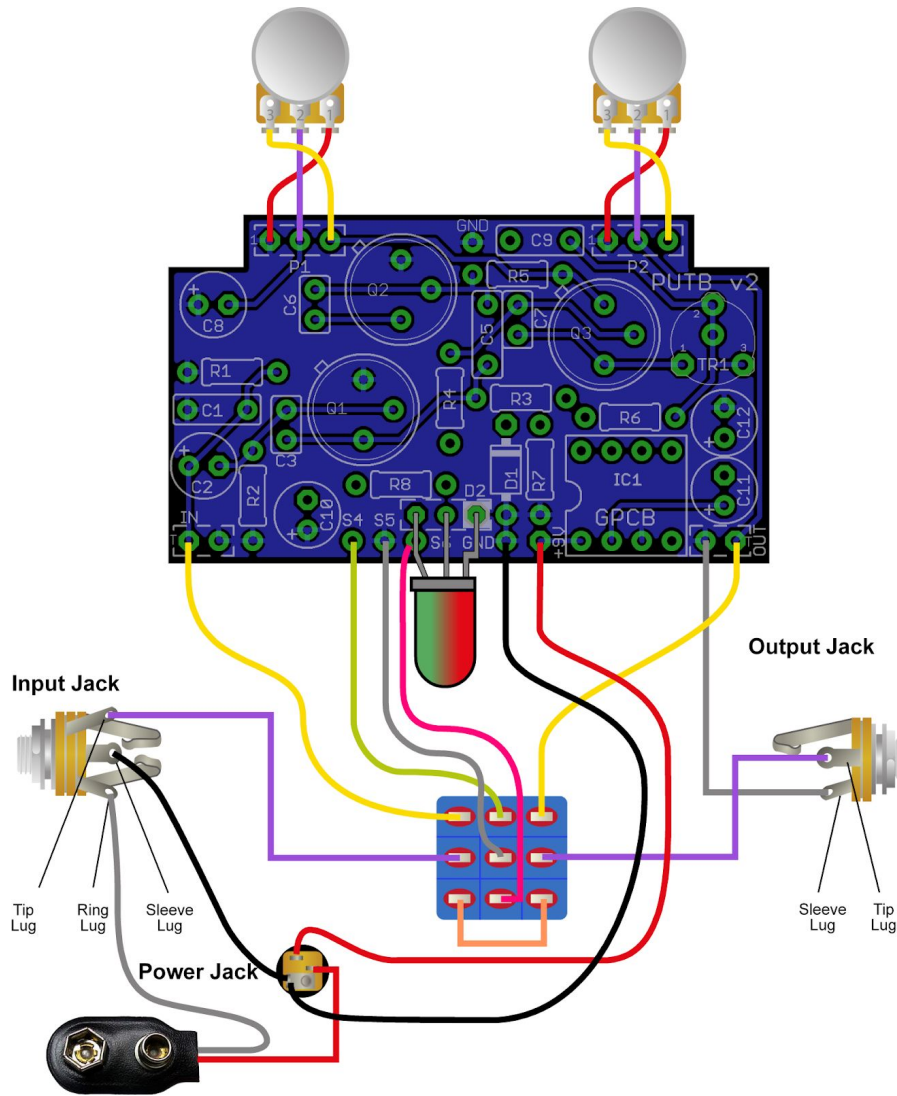

You may also choose to use a handy 3PDT Wiring Board from GuitarPCB in which case you can mount your LED to it and thus you will not need to install R8 or D2 on the Main Board or connect S4, S5 and S6.

